

### Experiment: Three Phase Measurements

1. Describe the different methods of three phase measurements for balanced three phase load & Unbalance three Phase loads?
2. Compare the pros & cons of the methods you described in question 1?
3. Derive the equation of total load power in a wye (Y) configuration for two watt meter method?