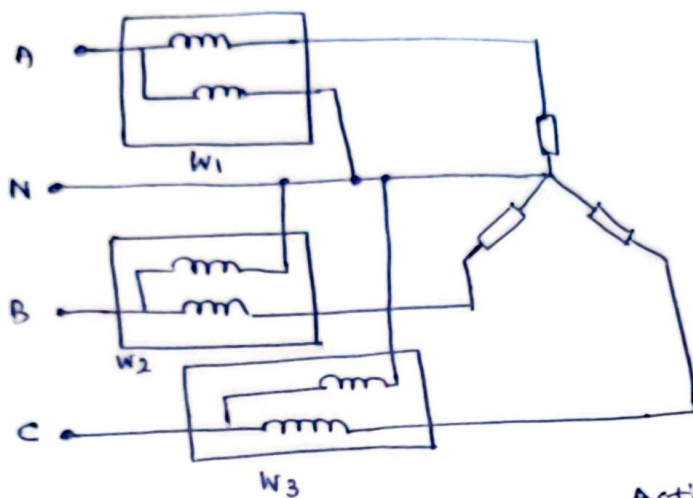


① Describe the different methods of three phase measurements for balanced three phase load & unbalanced three phase loads?

(i) Three-wattmeter method




- configuration: each wattmeter is connected to a line (A, B, C) with common neutral

- Used for - balanced and unbalanced loads

- this configuration requires a neutral connection.

Active power $\rightarrow P = W_1 + W_2 + W_3$

(ii) Two-wattmeter method

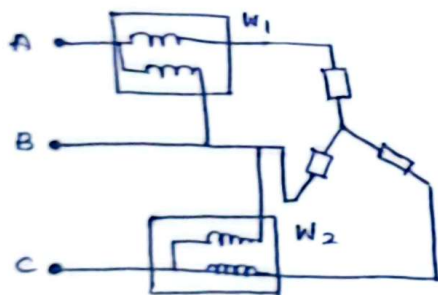

- configuration: wattmeters are connected between two lines.

- Used for \rightarrow balanced loads system: star or delta
- unbalanced loads system: only in 3-wire systems (no neutral)


Active power = $W_1 + W_2$

Reactive power = $\sqrt{3} (W_2 - W_1)$

$$\phi = \tan^{-1} \left(\frac{\sqrt{3} (W_2 - W_1)}{(W_1 + W_2)} \right)$$

$\cos \phi \rightarrow$ power factor.

(iii) One-wattmeter method.

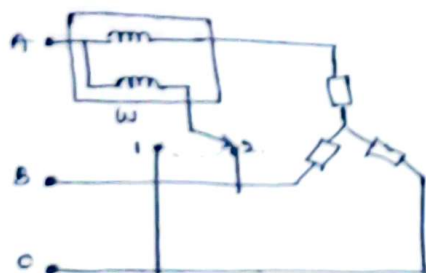

- configuration: one wattmeter connected and reading taken with switching connections.



- Used only for balanced loads.

Active power = $W_1 + W_2$

② Compare the pros & cons of the methods you described in q1?

method	Pros	Cons.
Three-wattmeter.	<ul style="list-style-type: none"> • Suitable for 4-wire systems with neutral • Accurate for both balanced & unbalanced systems. 	<ul style="list-style-type: none"> • Requires 3 wattmeters. • Need access to the neutral point • Complex wiring.
Two-wattmeter	<ul style="list-style-type: none"> • Works for both balanced and unbalanced loads. (In 3-wire systems) • Can be used to calculate power factor. • Does not require neutral • Only two wattmeters required. 	<ul style="list-style-type: none"> • Accuracy reduce at lower power factors. • Not suitable for 4-wire systems.
One-wattmeter	<ul style="list-style-type: none"> • Economical, only needed one wattmeter. • Simple setup for balanced loads. 	<ul style="list-style-type: none"> • Only works for balanced loads. • Required switching for full measurement.

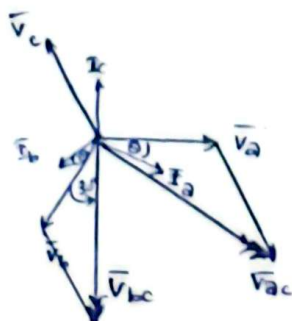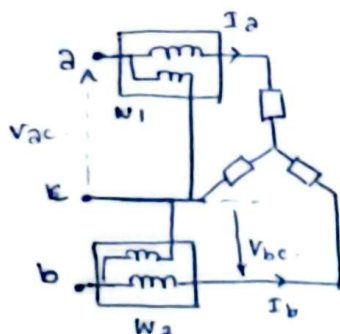③ Derive the equation of total load power in a wye (Y) configuration for two-wattmeter method.



assume that reference is \bar{V}_a , and power factor is $\cos \theta$ (lagging).

$$W_1 = |\bar{I}_a| |\bar{V}_{ab}| \cos(30^\circ - \theta) \\ = I_L V_L \cos(30^\circ - \theta) \quad \text{--- ①}$$

$$W_2 = |\bar{I}_b| |\bar{V}_{bc}| \cos(30^\circ + \theta) \\ W_3 = I_L V_L \cos(30^\circ + \theta) \quad \text{--- ②}$$

$$\text{①} + \text{②} \Rightarrow W_1 + W_2 = I_L V_L [\cos(30^\circ - \theta) + \cos(30^\circ + \theta)] \\ = I_L V_L [2 \cos 30^\circ \cos \theta] \\ \underline{W_1 + W_2 = \sqrt{3} I_L V_L \cos \theta}$$

$$\text{Active power} = \sqrt{3} V_L I_L \cos \theta$$

$$\therefore \text{Active power} = \underline{W_1 + W_2}$$

03/07
P